

190101085
SIDDHARTH CHARAN

Q.1 We need to design counter which count the following sequence & repeat:-
 $\Rightarrow (5, 7, 2, 5, 6, 3, 1, 4)$ & repeat it.

Q_2	Q_1	Q_0	P_2	P_1	P_0
0	0	0	1	0	1
0	0	1	1	1	1
0	1	0	0	1	0
0	1	1	1	0	1
1	0	0	1	1	0
1	0	1	0	1	1
1	1	0	0	0	1
1	1	1	1	0	0

Q_1, Q_0	00	01	11	10
Q_2				
0	1	1	1	0
1	1	0	1	0

$$P_2 = \overline{Q_1} \overline{Q_0} + \overline{Q_2} Q_0 + Q_1 Q_0$$

Q_1, Q_0	00	01	11	10
Q_2				
0	0	1	0	1
1	1	1	0	0

$$P_2 = \overline{Q_1} Q_0 + Q_2 \overline{Q_1} + \overline{Q_2} \overline{Q_0} \overline{Q_0}$$


Q_1, Q_0	00	01	11	10
Q_2				
0	1	0	1	0
1	0	1	0	1

$$P_0 = \overline{Q_2} \overline{Q_1} + Q_2 Q_1 \overline{Q_0} + \overline{Q_2} Q_0$$

190101005

SIDDHARTH CHARRAN

DATE
PAGE

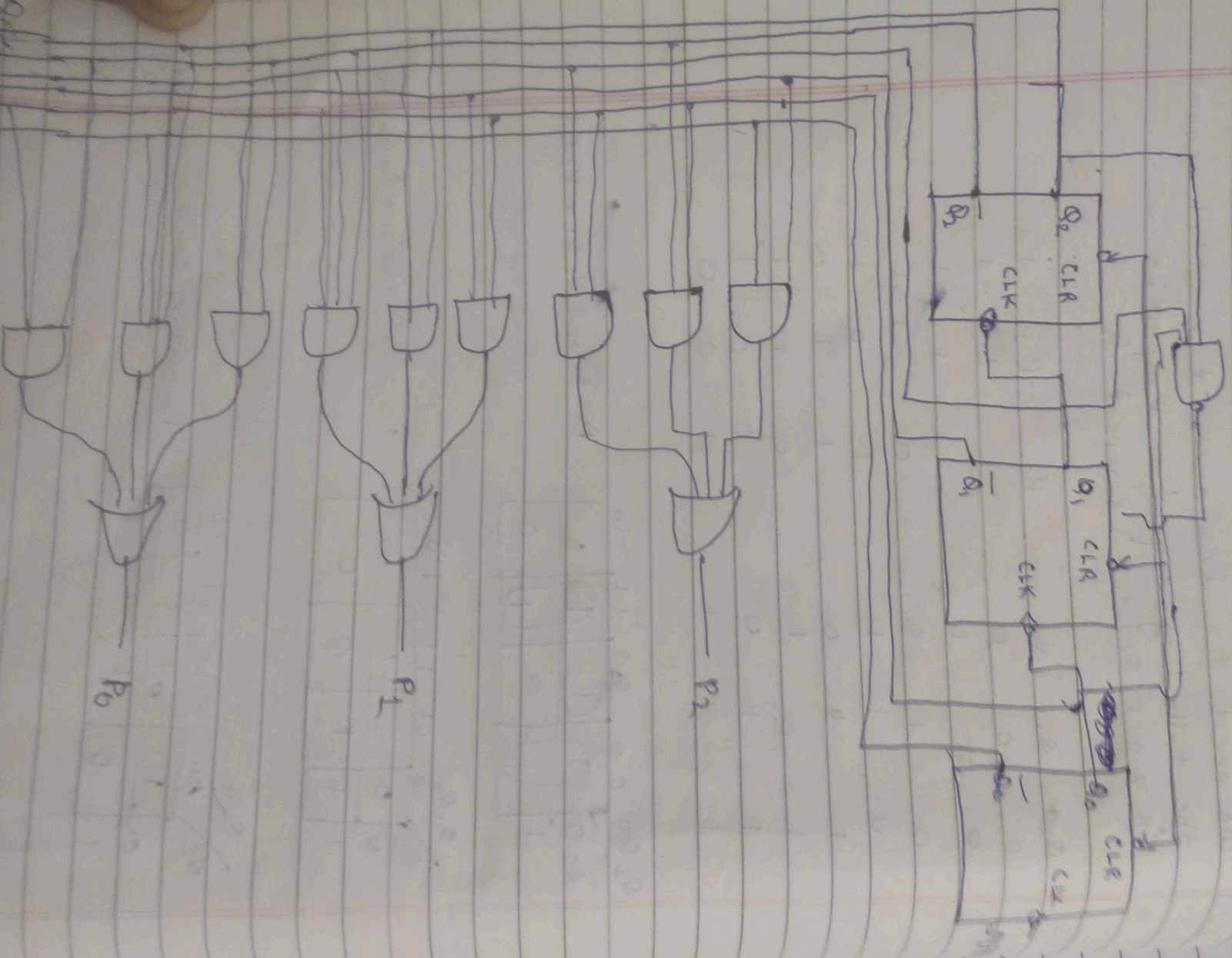

190101085
SIDHARTH CHARAN

② We need to design a 4-bit register to support following eight functions :-

- i. Parallel input
- ii. Parallel output
- iii. Left shift with rotate
- iv. Right shift with rotate
- v. Left shift with left serial in, serial out
- vi. Right shift with right serial in, serial out
- vii. Complement the bits
- viii. Swap bits

⇒ As there are 8 tasks, we need to use a 3x8 MUX.

⇒ We will use 4-0 Flip flops, As there are 4 bits.

S ₂	S ₁	S ₀	Parallel Input
0	0	0	Parallel Output
0	0	1	Left rotation
0	1	0	Right rotation
0	1	1	Left shift with serial in
1	0	0	Right shift with serial in
1	0	1	Complement the bits
1	1	0	swap bits.
1	1	1	

19010 1085

SIDDHARTHA CHARAN

