

190101085

(c)

Tab form

$P_2, P_1, P_0$

0	0	0
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1

X

0 - X X X X 0 - 0 F

NS

0 0 0  
0 0 1  
0 1 0  
0 0 1  
1 0 0  
1 0 0  
0 0 0  
1 0 0  
0 0 0  
1 1 0

Y


0 0 1 1 1 1 1 0 0

(d)

SIDDHARTH CHARAN

190101085

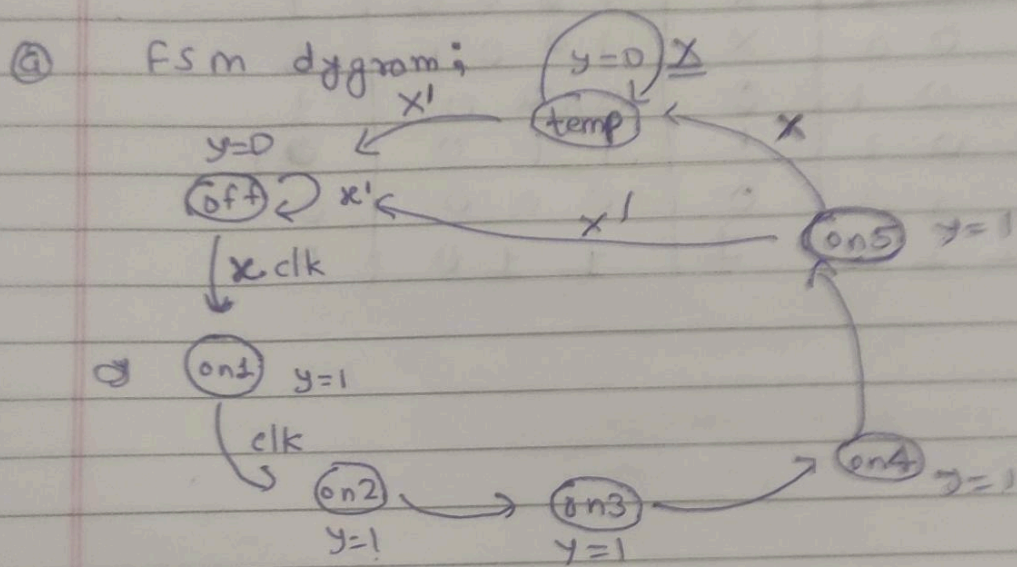
- Q.1 We are asked to design a Moore FSM with  
inputs  $\Rightarrow x$   
output  $\Rightarrow y$   
if  $x=0$ , return to start  
if  $x=1$ ,  $y$  should become 1 for five clocks  
and return to 0 after that



- For verifying these properties:-



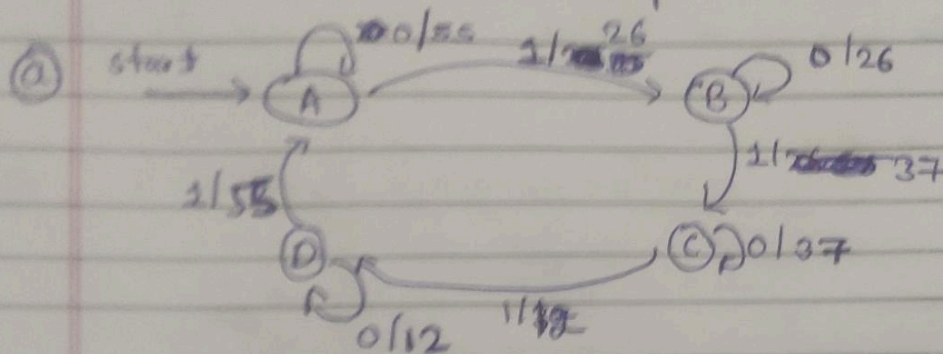- Q.1) We need to design a Mealy type FSM for counter which count 5, 5, 26, 37, 12 & repeat; whenever  $X=1$ , otherwise we need to hold to counter value to present state.



- Q.2) We can state it like this:-


	P S		X		y (output)						
	P <sub>5</sub>	S			P <sub>5</sub>	P <sub>4</sub>	P <sub>3</sub>	P <sub>2</sub>	P <sub>1</sub>	P <sub>0</sub>	
A	0	0	0		1	0	1	0	1	1	1
B	0	1	0		0	1	1	0	1	0	
C	1	0	0		0	0	0	1	0	1	
D	1	1	0		0	0	1	1	0	0	
	1	0	1		1	1	0	1	1	1	
	0	0	1		0	1	1	0	1	0	
	0	0	1		1	0	0	1	0	1	
	1	0	1		0	0	1	1	0	0	

190101025  
SIDDHARTH CHARAN

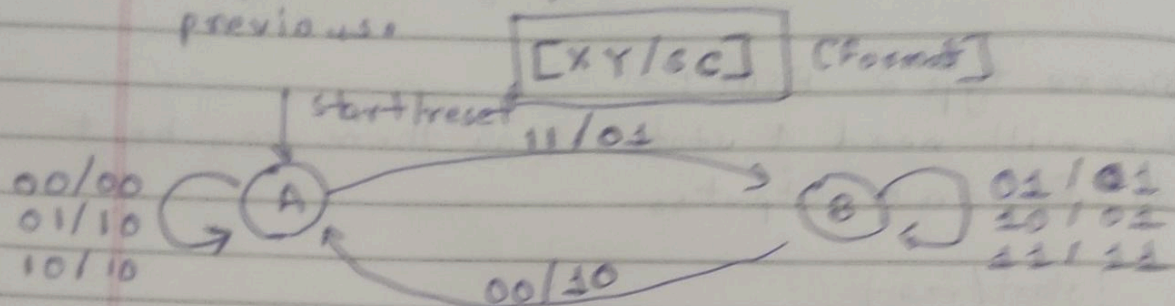(ii) Malay Implementation -

We need only two states for it.

⇒ input and output formats are same as previous.



Here;

A state is when carry is 0.

B is when carry is 1.



190101085

SIDDHARTH CHARAN

Q. 3

Given :


X and Y  $\rightarrow$  inputs

S and C  $\rightarrow$  outputs

We need to draw mealy & moore FSM for

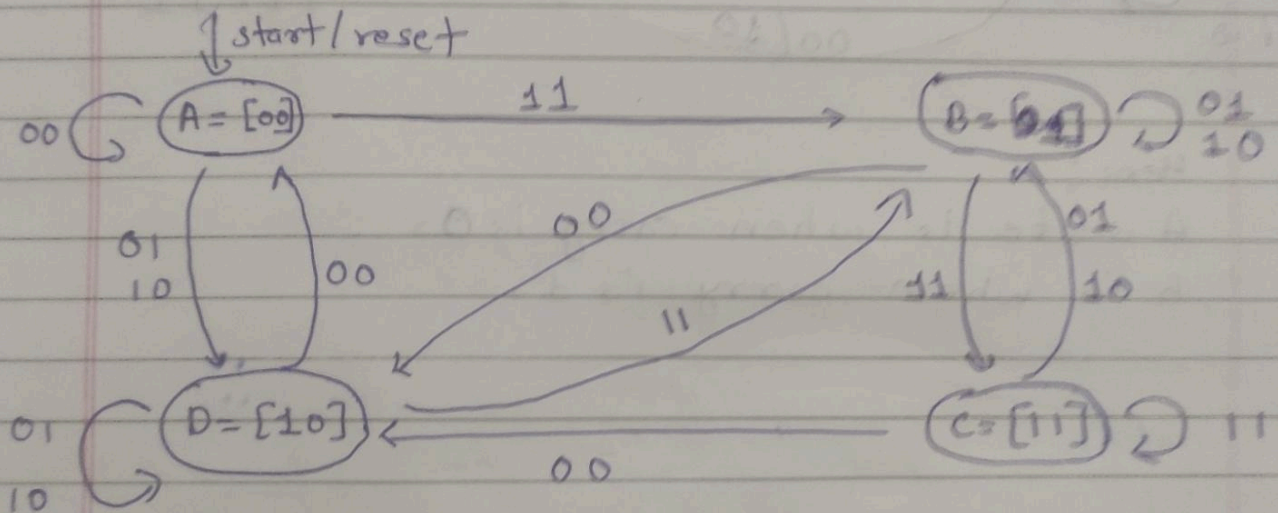(i) Moore type FSM :-

We will need 4 states as there can be 4 different outputs.



Input Format  $\Rightarrow \{x, y\}$

Output Format  $\Rightarrow [s, c]$

at state A  $\Rightarrow [00]$

B  $\Rightarrow [01]$

C  $\Rightarrow [11]$

D  $\Rightarrow [10]$