

CS221-Assignment

Due date for submission 31 Oct 2020

Submission procedure: Written/typed upto four pages and submit/upload PDF document (scanned copy of written) on to CS221 MS Team assignment upload

1. Design counter which count the following sequence and repeat. *(you should use minimum number of flipflop, and also you are allowed to any extra circuitry if you wish other than required number flip-flops)*

5, 7, 2, 5, 6, 3, 1, 4, 5, 7, 2, 5, 6, 3, 1, 4, 5, 7, 2, 5, 6, 3, 1, 4,...

2. Design a 4-bit register to support following eight functions and draw a neat diagram for your designed register
 - i. Parallel input
 - ii. Parallel output
 - iii. Left shift with rotate
 - iv. Right shift with rotate
 - v. Left shift with left serial in, serial out
 - vi. Right shift with right serial in, serial out
 - vii. Complement the bits
 - viii. Swap bits (0th bit goes to 3rd bit, 3rd bit goes to 0th bit, 1th bit goes to 2th bit and 2nd bit goes to 1th bit)