

CS221-Assignment

Post Mid Sem Assignment No: 2

Due date for submission : 8 Nov 2020

Submission procedure: Written/typed upto four pages and submit/upload PDF document (scanned copy of written) on to CS221 MS Team assignmentupload

=====

1) Design a 3 bit gray counter which counts 000, 001, 011, 010, 110, 111, 101, 100, and repeat. The counter output $Z=1$ when the value of the counter is 0. The counter counts when the input value is $X=1$.

- Draw Moore FSM diagram for the specified counter.
 - Implement the counter based on Moore FSM using D-FFs (No need to draw circuit diagram of the counter, but required to next state Boolean function input for inputs of the FFs)
 - Implement the counter based on Moore FSM using JK-FFs
- Draw Melay FSM diagram for the specified counter
 - Implement the counter based on Moore FSM using T-FFs
 - Implement the counter based on Moore FSM using RS-FFs

2) A long sequence of pulses entering a synchronous sequential circuit which is required to produce an output $Z=1$, whenever sequence 1111 occurs. Overlapping sequences are accepted. For example, if the input is 01011111, the required output is 00000011. Design the circuit of the system.

- Draw Moore FSM diagram for the same.
- Implement the same using D-FFs (No need to draw circuit diagram of the counter, but required to next state Boolean function input for inputs of the FFs)