


130101085

SIDDHARTH CHARAN

Q. ① Given: $Y = X_1 X_2' + (X_1 + X_2) Y$
 $(Y = X_1 X_2' Y + X_1 X_2' Y' + X_1 X_2 Y + X_1' X_2' Y)$

and $z = Y$

We can obtain logic diagram as follow

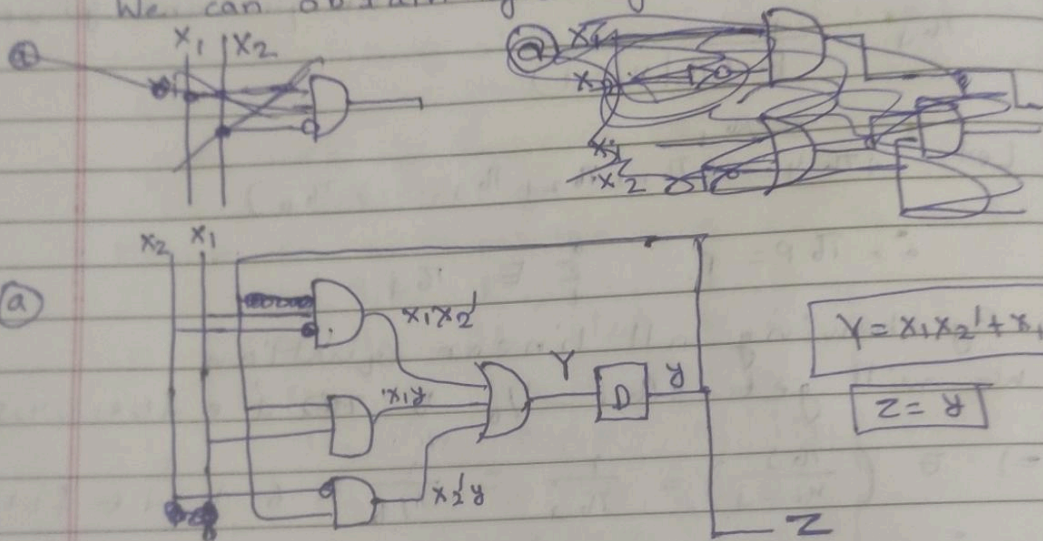

(b) We can easily derive transition table & output map as follow:-

		$X_1 X_2$			
(i)	Y	00	01	11	10
	0	0	0	0	1
	1	1	0	1	1

		$X_1 X_2$			
(ii)	Z	00	01	11	10
	0	0	0	0	0
	1	1	1	1	1

190101085

SIDDHARTH CHARAN

Hence we get


	Y, z			
	Y, z			
x_1, x_2	00	01	11	10
0	Ⓐ, 0	Ⓐ, 0	Ⓐ, 0	Ⓐ, 0
1	Ⓑ, 1	Ⓑ, 1	Ⓑ, 1	Ⓑ, 1

© We can give $Y=0$ name as state-A and $Y=1$ as state-B we get;

	State, output			
	Y, z			
x_1, x_2	00	01	11	10
PS				
0 A	Ⓐ, 0	Ⓐ, 0	Ⓐ, 0	Ⓐ, 0
1 B	Ⓑ, 1	Ⓑ, 1	Ⓑ, 1	Ⓑ, 1

⇒ We can get each state from any other state. So, we need not care about -- (i.e. don't care)

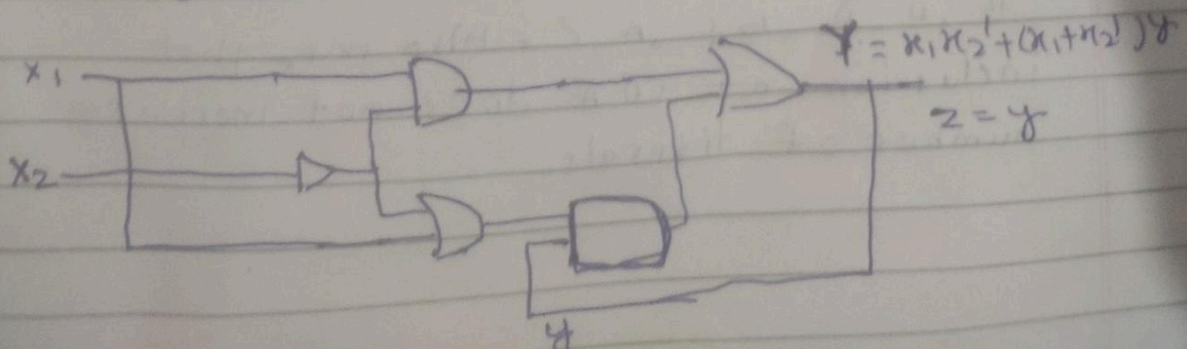note we can obtain part © in more efficient manner



A② We need to implement the following problem function without any hazards:-

$$F(a, b, c, d) = \Sigma(0, 2, 6, 7, 8, 10, 12)$$

Let us first try to draw the K-map

	00	01	11	10
00	0	1	3	2
01	4	5	6	7
11	12	13	15	14
10	8	9	11	10

- Groups:-
- (i) $\bar{B} \bar{D} : (0, 2, 8, 10)$
 - (ii) $\bar{A} B C : (6, 7)$
 - (iii) $A \bar{C} \bar{D} : (3, 12)$

We have circled groups above

We get:-

$$F(A, B, C, D) = \bar{B} \bar{D} + \bar{A} B C + A \bar{C} \bar{D}$$

Now note that the literals we have are

$\bar{B}, \bar{D}, \bar{A}, B, C, A, \bar{C}$. Also note that inclusion of $C \bar{D} \bar{A}$ does not increase number of literals.

130101085

SIDHARTH CHAKRAVARTY

But it ensures no static hazards & hence glitching
we get :-

$$F(A, B, C, D) = \overline{B} \overline{D} + \overline{A} B C + A C \overline{D} + \overline{A} C D$$

(in sop form)

We can implement this as follows

