

CS221: Digital Design**Full Mark – 30****Time 40 min.**

| | | |
|----|---|----------------|
| 1. | <p>An asynchronous sequential circuit is described by the excitation function</p> $Y = x_1x_2' + (x_1 + x_2')y$ <p>and the output function</p> $z = y$ <p>(a) Draw the logic diagram of the circuit. (b) Derive the transition table and output map. (c) Obtain a two-state flow table.</p> | [2+(3+2)+3=10] |
| 2. | <p>Find a circuit that has no Static hazards and implements the Boolean function</p> $F(a,b,c,d) = \Sigma(0, 2, 6, 7, 8, 10, 12)$ | [10] |
| 3. | <p>Suppose you are given an asynchronous counter module (mod-8) i.e., it counts (0, 1, 2, 3, 4, 5, 6, 7).</p> <p>(a) How many such sequences are possible for a mod-n ($n \geq 2$) counter?</p> <p>(b) Use the asynchronous counter (Mod-8) to design a counter that counts the ordered sequence (1, 2, 3, 5, 4, 6, 0, 7). [Hints: - You can use other logic circuit elements such as and, or, not gates.]</p> | [2 + 8 = 10] |