

# IIT GUWAHATI, DEPT OF CSE

CS221 (Digital Design) Examination Module 9 (Based on ASM/Lec 33, 34, 35)

Date: 20<sup>th</sup> November 2020, Timing: 9.00AM to 9.45AM


Total Mark: 20

**Submission Procedure:** Submit PDF scan copy of handwritten answer sheet (mention your name and roll no in the sheet) to MS Team course examination link before 9.50AM of 20<sup>th</sup> November 2020.

- **Submission after 10.00AM of 20<sup>th</sup> Nov 2020 will not be accepted.**
- **If you have any issue with MS team upload then send email to me quickly (mentioning your Roll No, Exam 9 and attach the solution) before 10.15AM of 20<sup>th</sup> Nov 2020.**

1. [2+3+2+3 **Marks**] Given Serial Binary Adder as shown below.

 - a) Draw Mealy type FSM for serial binary adder, where serial binary adder has two primary inputs: X and Y, two outputs: S and C, and the carry output is feedback to input of the full adder through a D-flip flop as shown in the diagram.



- b) [2+2] Draw ASM chart for the corresponding to the Mealy FSM for the above serial binary adder. Identify all the ASM blocks of your ASM.
- c) Infer the data path required for the drawn ASM
- d) Design an ASM controller (mentioning all required control signals, input signals) for the same using a decoder (to identify all the different states) and other logic.
2. [4+2+4 **Marks**] Design a digital system which calculate sum of first N odd number. Your designed digital system should have input two input (a) go signal (1 bit) and (b) the value N (8-bit number). Outputs are ready/done signal and the sum (a 16-bit number).
- a) [2+2] Draw ASM chart for the above problem. Identify all the ASM blocks of your ASM.
- b) Infer the data path required for the drawn ASM.
- c) Design an ASM controller (mentioning all required control signals, input signals) for the same using a decoder (to identify all the different states) and other logic.